

$$U_{LH} = \frac{1}{xQ} \sqrt{1 + Q^2 \left(x - \frac{1}{x}\right)^2} E_m$$

$$U_{LH} = \frac{1}{\sqrt{\frac{1}{x^2 Q^2} + \left(1 - \frac{1}{x^2}\right)^2}} E_m$$

$$U_{LH} = \frac{1}{\sqrt{\frac{x}{Q^2} + (1-x)^2}} E_m \quad \text{on pose } x = \frac{1}{x^2}$$

$U_{LH}(\omega_{res}) = U_{LH}(\omega_x)$ correspond à :

$$\frac{x}{Q^2} + (1-x)^2 \text{ minimal}$$

$$\begin{aligned} \frac{dB}{dx} &= \frac{1}{Q^2} - 2(1-x) \\ &= \frac{1}{Q^2} - 2 + 2x = 0 \\ &\quad \uparrow \\ &\quad \omega = \omega_x \end{aligned}$$

$$\Rightarrow x = \frac{1}{2} \left(2 - \frac{1}{Q^2} \right) = 1 - \frac{1}{2Q^2} = \frac{1}{x^2}$$



$$x_{res} = \frac{1}{\sqrt{1 - \frac{1}{2Q^2}}} = \frac{\omega_x}{\omega_0}$$

$$\omega_x = \frac{\omega_0}{\sqrt{1 - \frac{1}{2Q^2}}} > \omega_0$$

à condition que $\frac{1}{x^2} > 0$!!!
 $1 - \frac{1}{2Q^2} > 0 \quad Q > \frac{1}{\sqrt{2}}$

Il y a résonance en tension pour ω_x si $Q > \frac{1}{\sqrt{2}}$ dans la résonance a lieu pour $\omega_x > \omega_0$ sachant que $\omega_x \geq \omega_0$

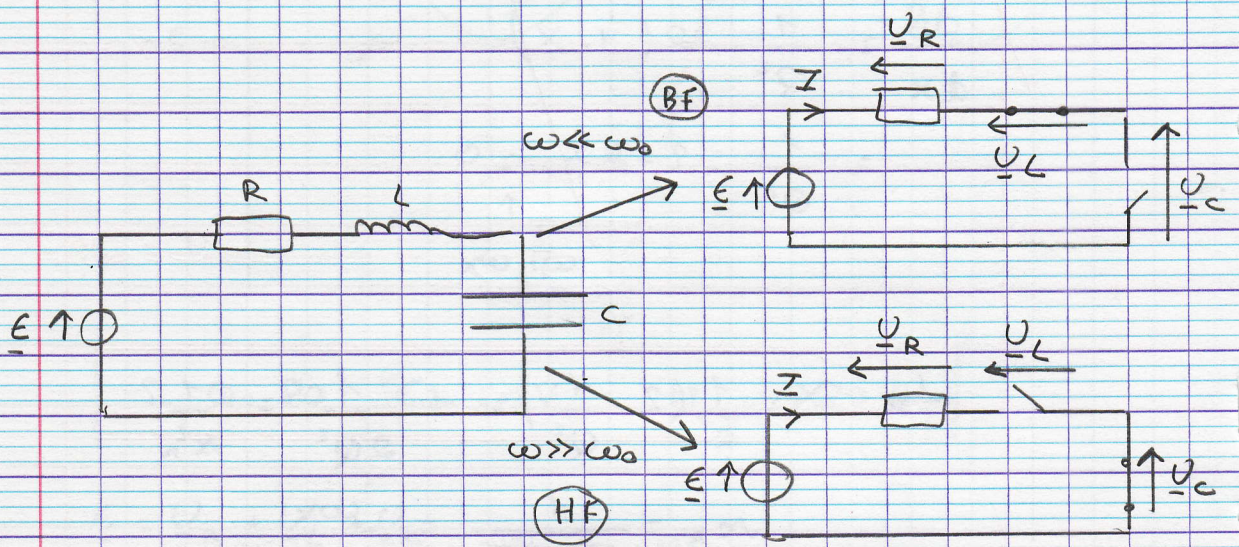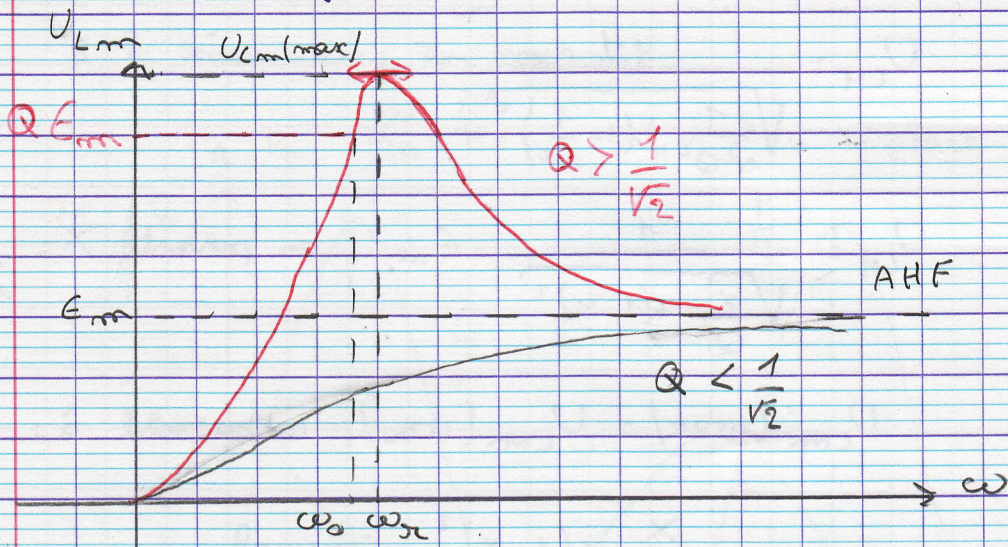
$$U_{L_{max}} = \frac{E_m}{\sqrt{\frac{1}{x^2 Q^2} + \left(1 - \frac{1}{x^2}\right)^2}} = \frac{Q x E_m}{\sqrt{1 + Q^2 \left(x - \frac{1}{x}\right)^2}}$$



(BF) $I \rightarrow 0 \Rightarrow U_R \rightarrow 0$
 $E = U_R + U_L + U_c$
 $U_L \rightarrow 0$ } $U_c \rightarrow E$

(HF) $I \rightarrow 0 \Rightarrow U_R \rightarrow 0$
 $E = U_R + U_L + U_c$
 $U_c \rightarrow 0$ } $U_L \rightarrow E$

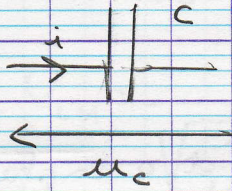φ^N de surtension aux bornes du Condensateur:



$$u_c = U_{cm} \cos(\omega t + \varphi_c)$$

$$\rightarrow u_c = U_{cm} e^{j(\omega t + \varphi_c)}$$

$$\rightarrow u_c = \underline{U}_c e^{j\omega t} \quad \text{avec} \quad \underline{U}_c = U_{cm} e^{j\varphi_c}$$

$$\text{or } \underline{U}_c = \frac{1}{j c \omega} \underline{I} \quad (*)$$

$$\text{d'où } |\underline{U}_c| = \left| \frac{1}{j c \omega} \right| |\underline{I}|$$

$$U_{cm} = \frac{1}{c \omega} I_{\text{rms}}$$

Surtension pour $\omega = \omega_0$

on est à la résonance en courant

$$\begin{cases} I_{\text{rms}}(\omega_0) = I_{\text{rms}}(\text{max}) = \frac{E_{\text{rms}}}{R} \\ \frac{1}{c \omega} = \frac{1}{c \omega_0} = Q R \end{cases}$$

$$Q = \frac{1}{R C \omega_0}$$

$$\rightarrow U_{cm}(\omega_0) = Q R \frac{E_{\text{rms}}}{R}$$


$$U_{cm}(\omega_0) = Q E_{\text{rms}}$$

$$(*) \rightarrow \arg(\underline{U}_c) = \arg\left(\frac{1}{j c \omega}\right) + \arg(\underline{I})$$

$$\varphi_c = -\frac{\pi}{2} + \varphi_i$$

en $\omega = \omega_0$ $\varphi_i = 0$ i en phase avec e à la résonance
 $x = 1$ en intensité

à la résonance en courant:

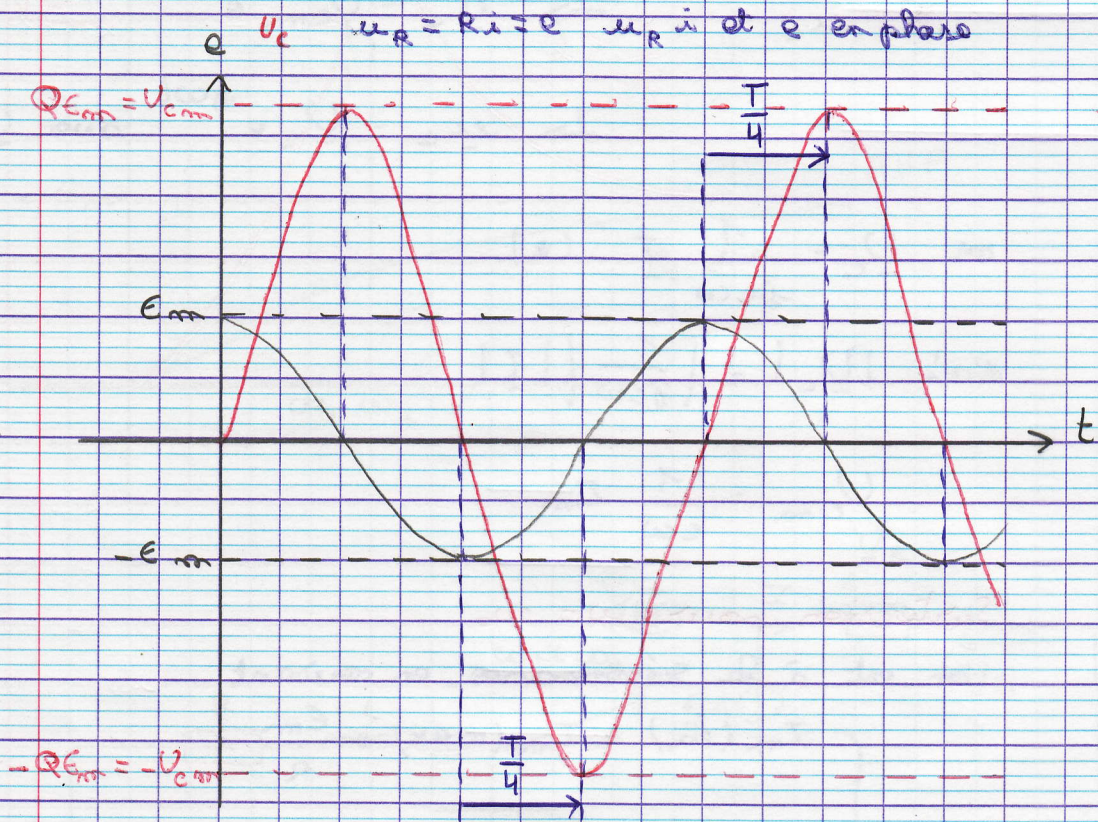

u_c est en quadrature retard de phase par à $e(t)$

Si $Q = 80$ $E_m = 1V$ $V_{cm} = 80V!$

$$\underline{E} = \underline{U}_R + \underline{U}_L + \underline{U}_C$$

$$= \underline{U}_R + E_m Q (e^{j\varphi_L} + e^{j\varphi_C})$$

$$\rightarrow = \underline{U}_R + E_m Q (j - j)$$

$u_c + u_L = 0$ $\forall t$ pour $\omega = \omega_0$

$\omega = \omega_0$ $\varphi_C = -\frac{\pi}{2}$ $\varphi_L = \frac{\pi}{2}$

$\forall t$ $u_R = e$ car $\underline{U}_R = R I_m e^{j\varphi_i} = R I_m$
 $\varphi_i = 0$

\rightarrow cf Polycop : Q^N de résonance en tension aux bornes de C.